

Project Report

Name:Sumaiya Chowdhury

ID:1711072642

Section:03

Course:CSE 332

I have made a 18 bit datapath design

ISA instruction:

00881:It is an OR operation where destination register is 00001,one source register is 00100,another source register is 00010 and opcode is 000

08881:It is a NOR operation where destination register is 00001,one source register is 00100,another source register is 00010 and opcode is 001


10881:It is an add or subtract operation where destination register is 00001,one source register is 00100,another source register is 00010 and opcode is 010.If we put 0 in B invert, it will perform add operation and if we put 1 in B invert,it will perform subtract operation

For immediate value,I have put load,store,select and clear in the ROM.Whenever we want to load or store a value,I will use the accessed primary memory.We can use an immediate value using it also


Screenshot:

Sub circuits:


1 bit alu

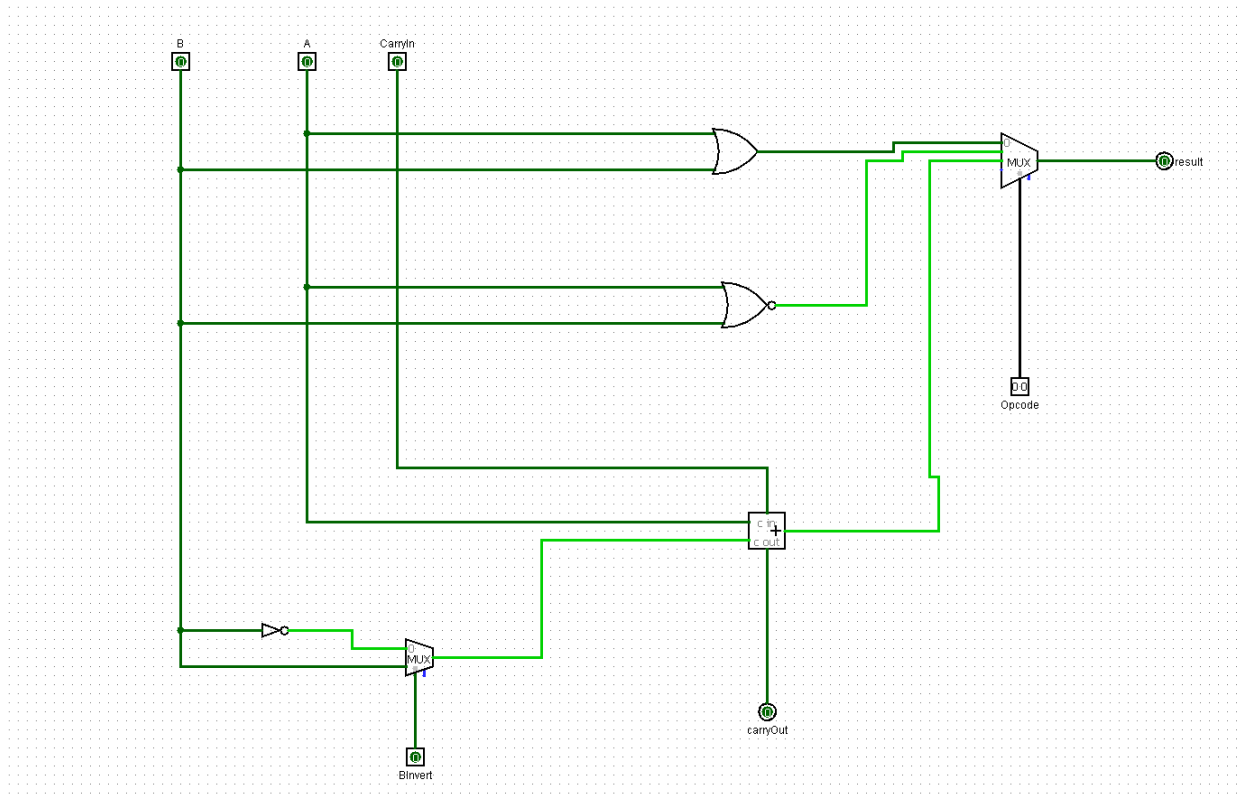

18 bit ALU

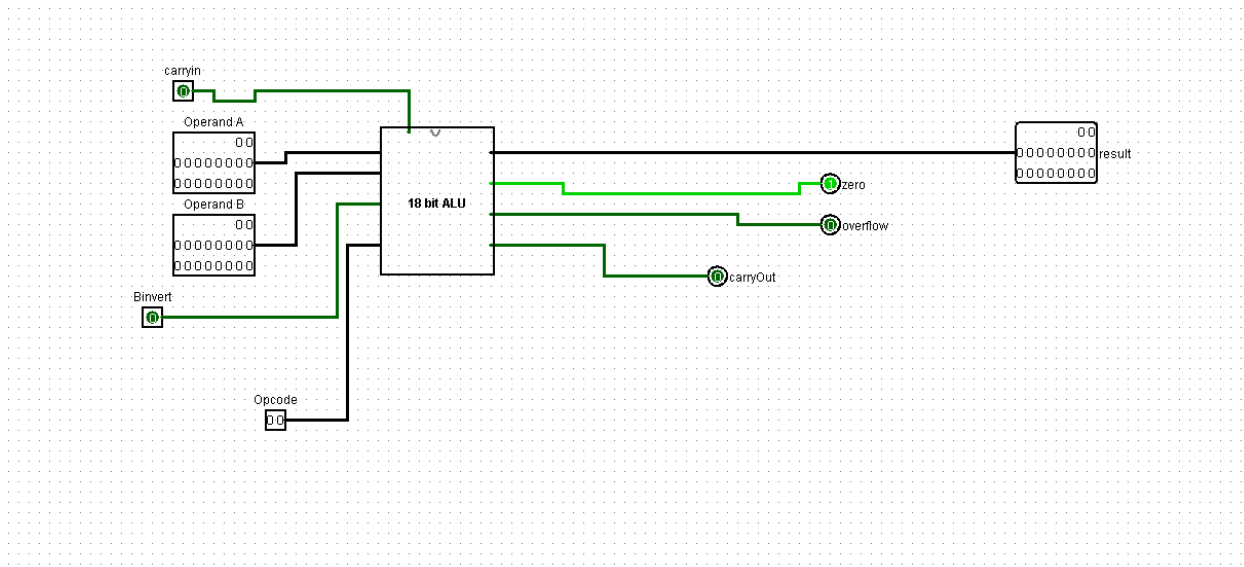


18 bit register file

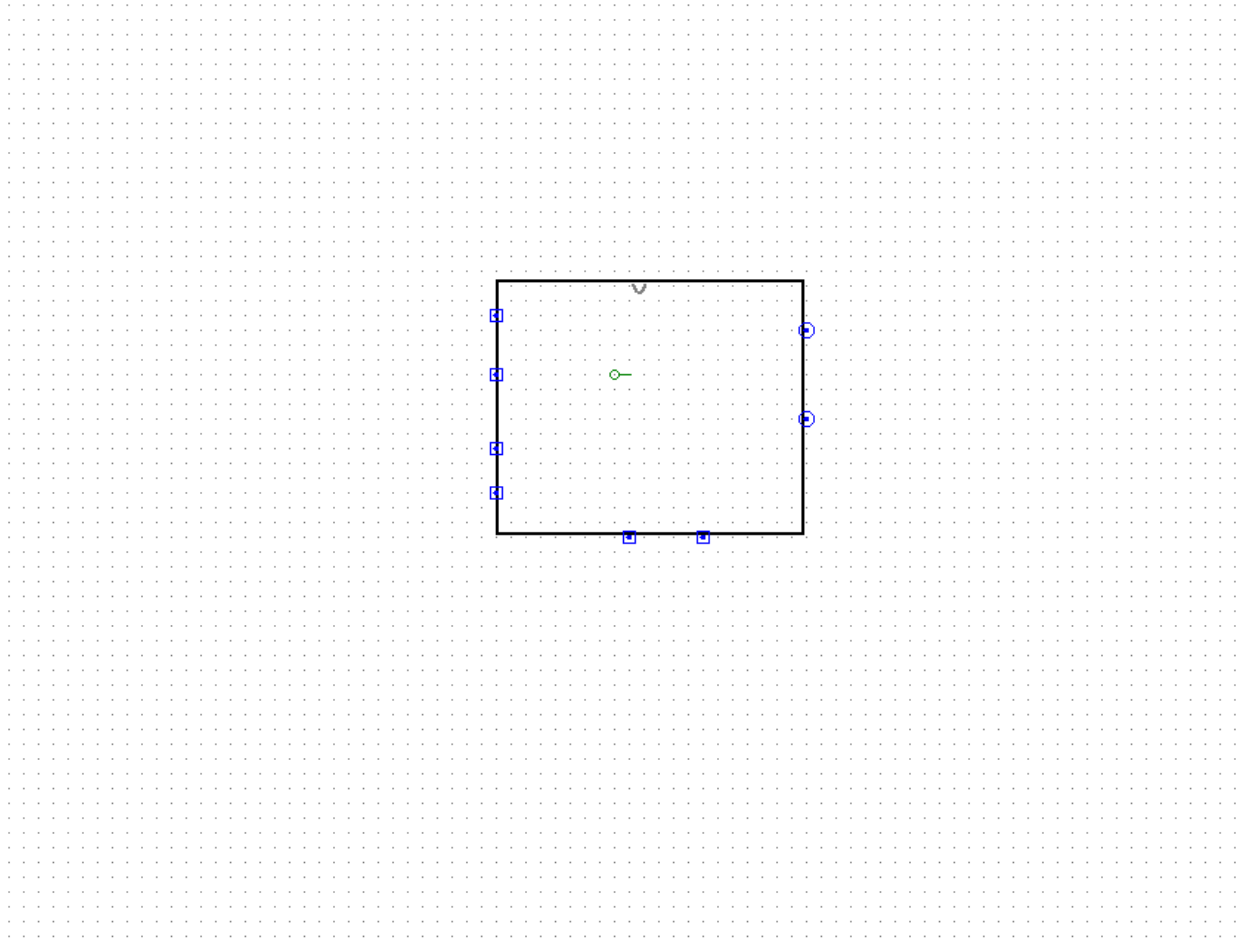

Main circuit:

For or

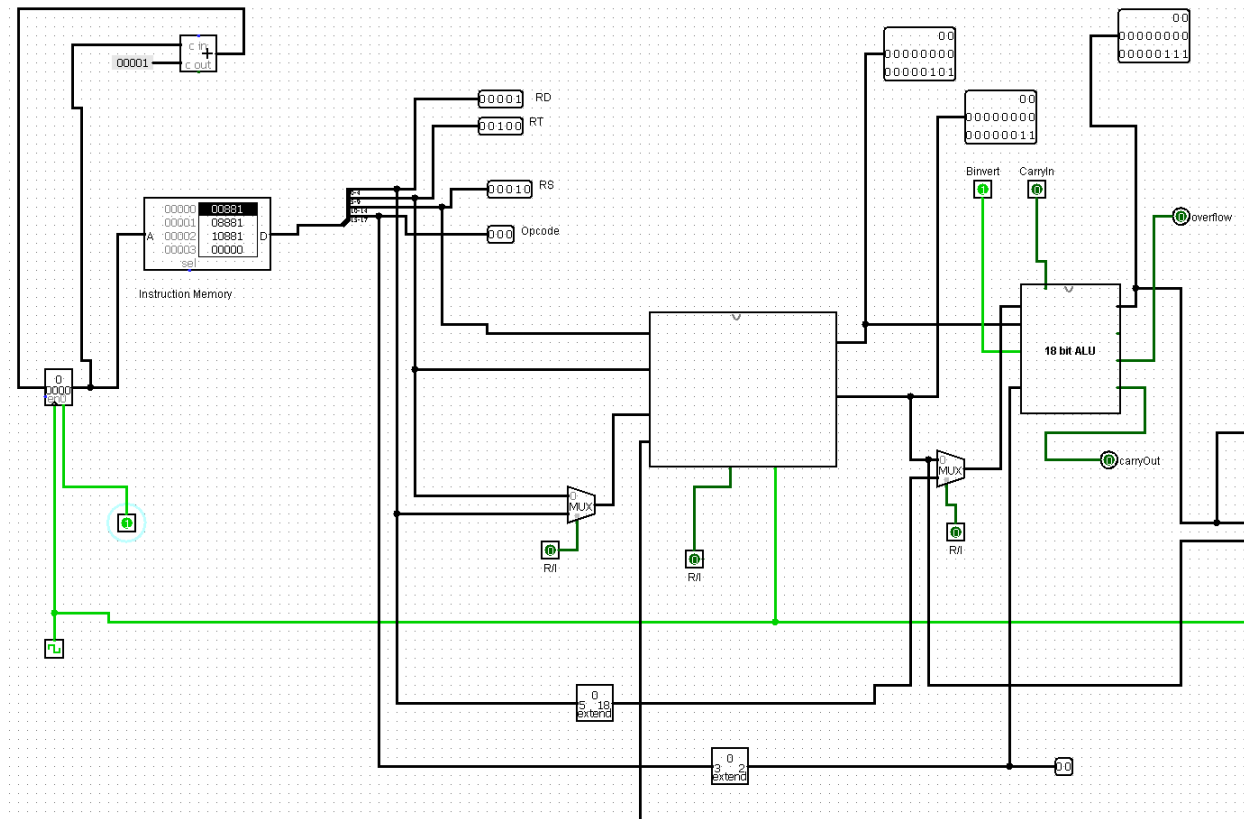


For NOR



For sub:



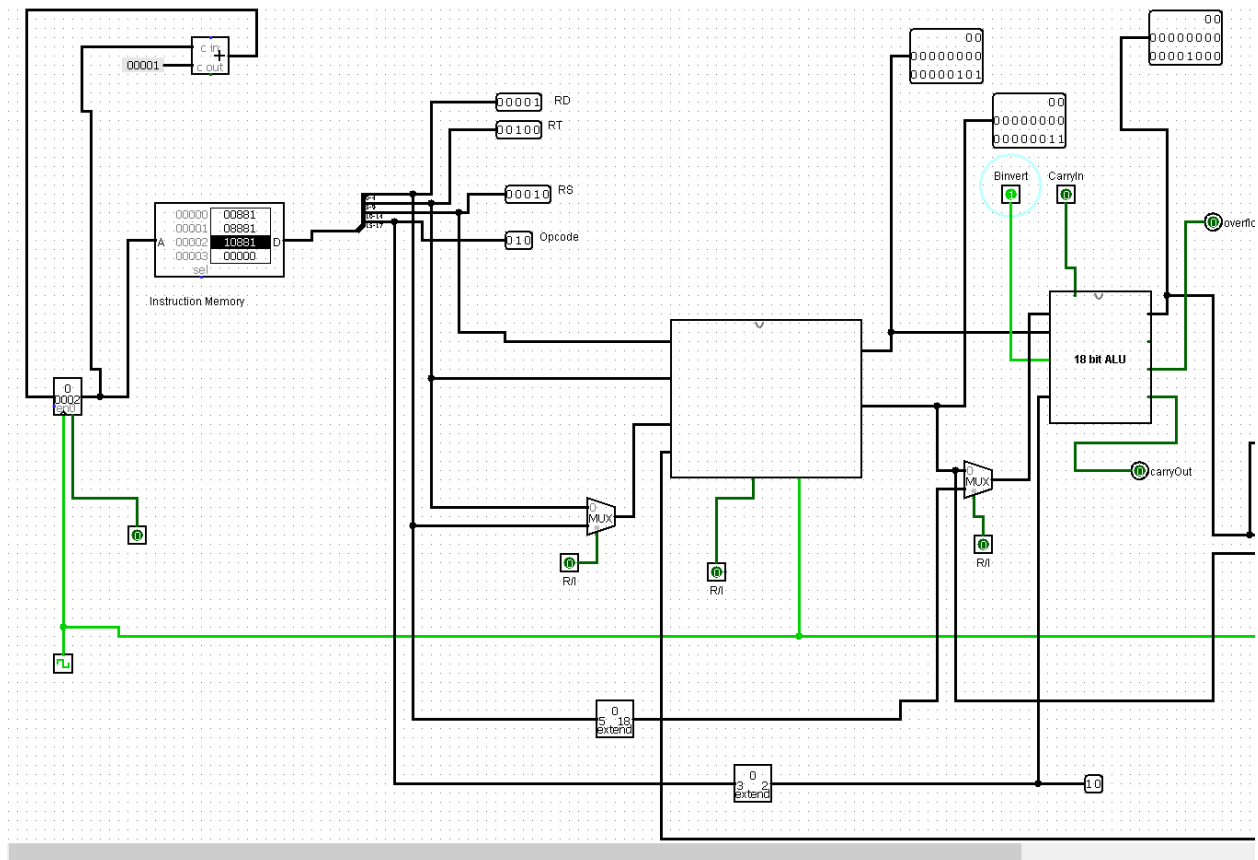

To write that add result in the register

